
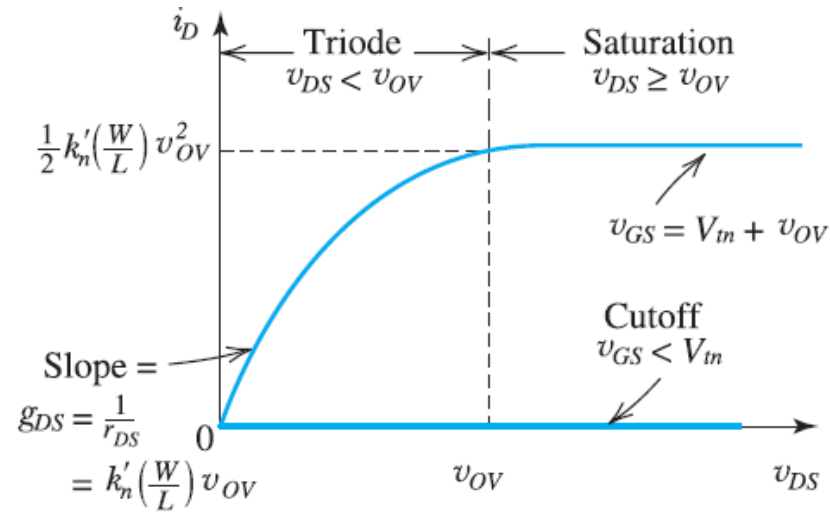


# Modes of Operation

## NMOS

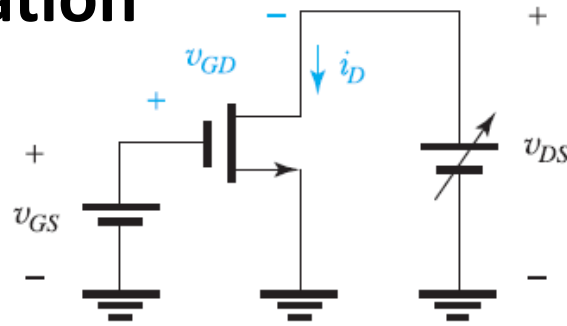

- $v_{GS} < V_{tn}$  : no channel; transistor in cutoff;  $i_D = 0$
- $v_{GS} = V_{tn} + v_{OV}$  : a channel is induced; transistor operates in the triode region or the saturation region depending on whether the channel is continuous or pinched off at the drain end;

### Triode Region

Continuous channel, obtained by:

$$v_{GD} > V_{tn}$$

or equivalently:

$$v_{DS} < v_{OV}$$

Then,

$$i_D = k'_n \left( \frac{W}{L} \right) \left[ (v_{GS} - V_{tn}) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

or equivalently,

$$i_D = k'_n \left( \frac{W}{L} \right) \left( v_{OV} - \frac{1}{2} v_{DS} \right) v_{DS}$$

### Saturation Region

Pinched-off channel, obtained by:

$$v_{GD} \leq V_{tn}$$

or equivalently:

$$v_{DS} \geq v_{OV}$$


Then

$$i_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (v_{GS} - V_{tn})^2$$

or equivalently,

$$i_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) v_{OV}^2$$

## $i_D$ vs $v_{DS}$ curves

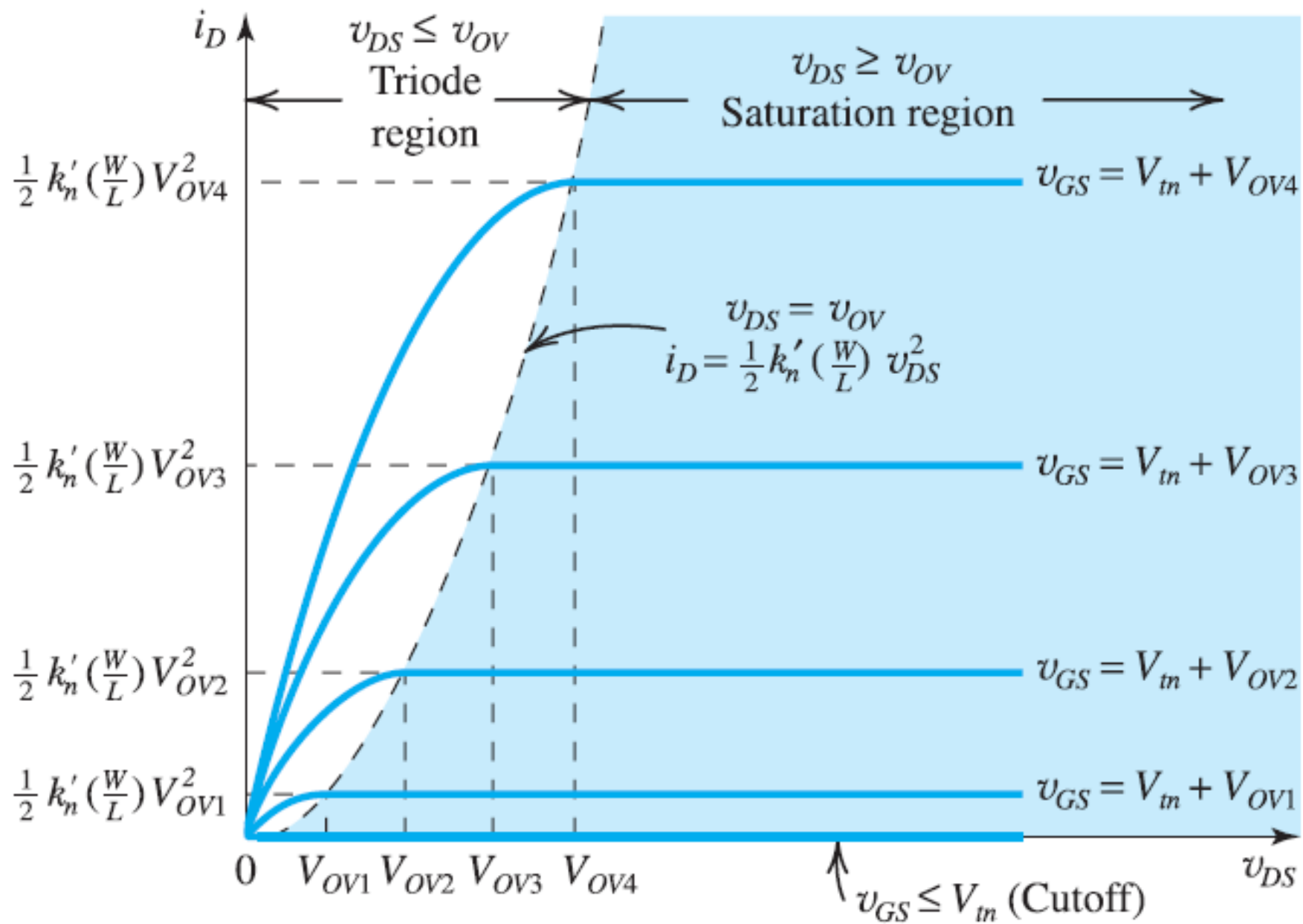

The  $i_D$ - $v_{GS}$  Characteristic




# Voltage-controlled current source

Saturation current

$$i_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (v_{GS} - V_{tn})^2$$


$$i_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) v_{ov}^2$$

## $i_D$ vs $v_{GS}$ curve

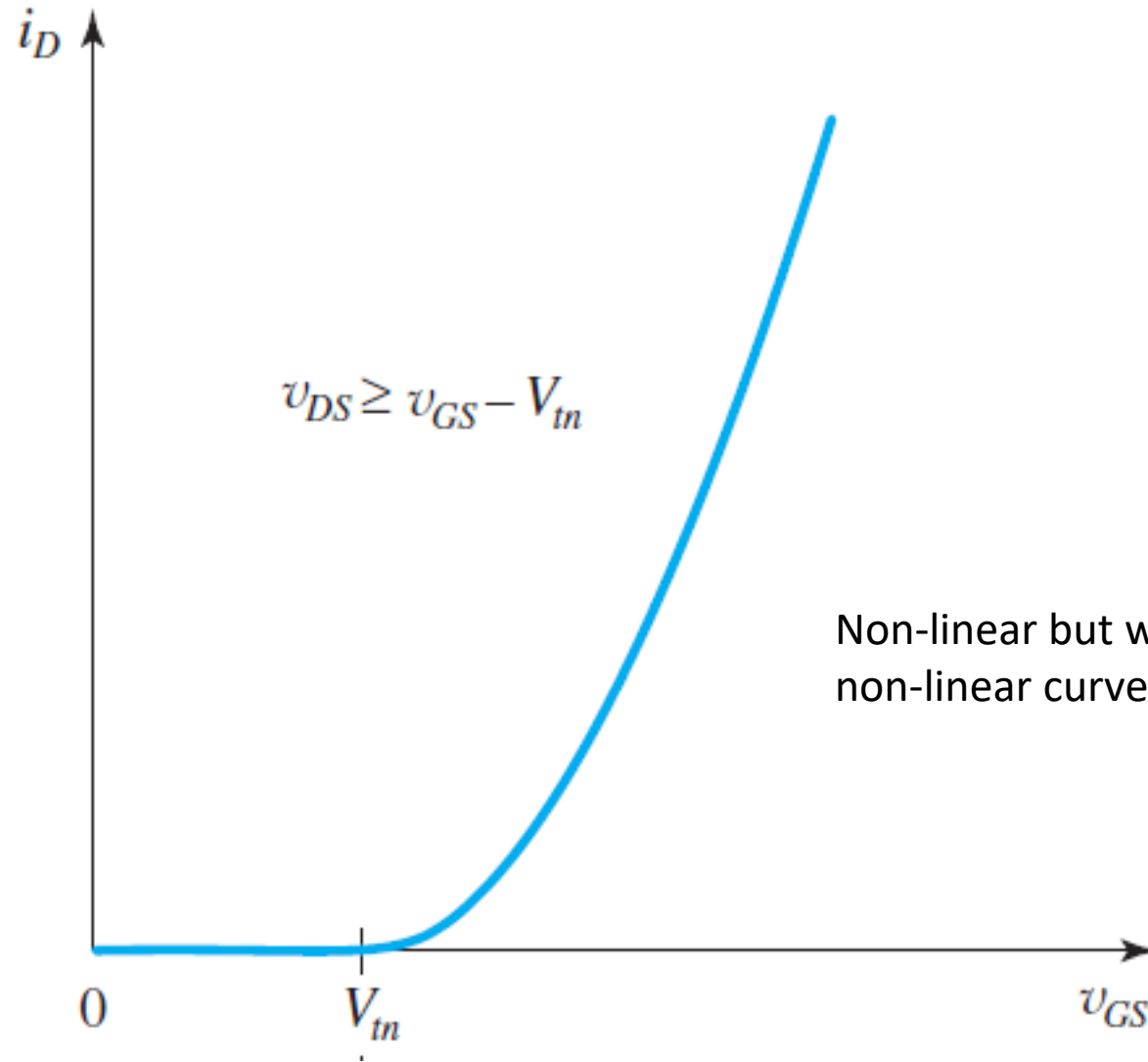

Non-linear but we know what to do with non-linear curves


# Large-Signal Model

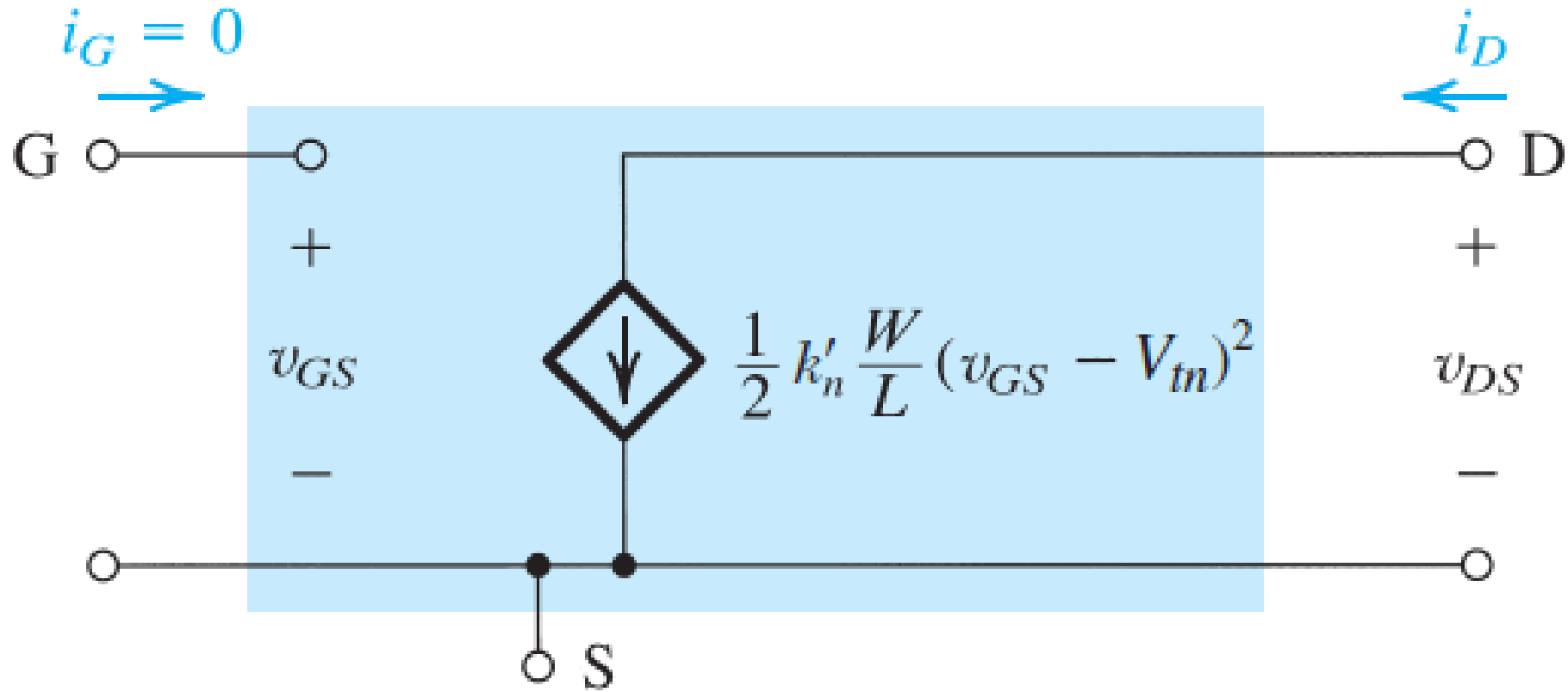


However
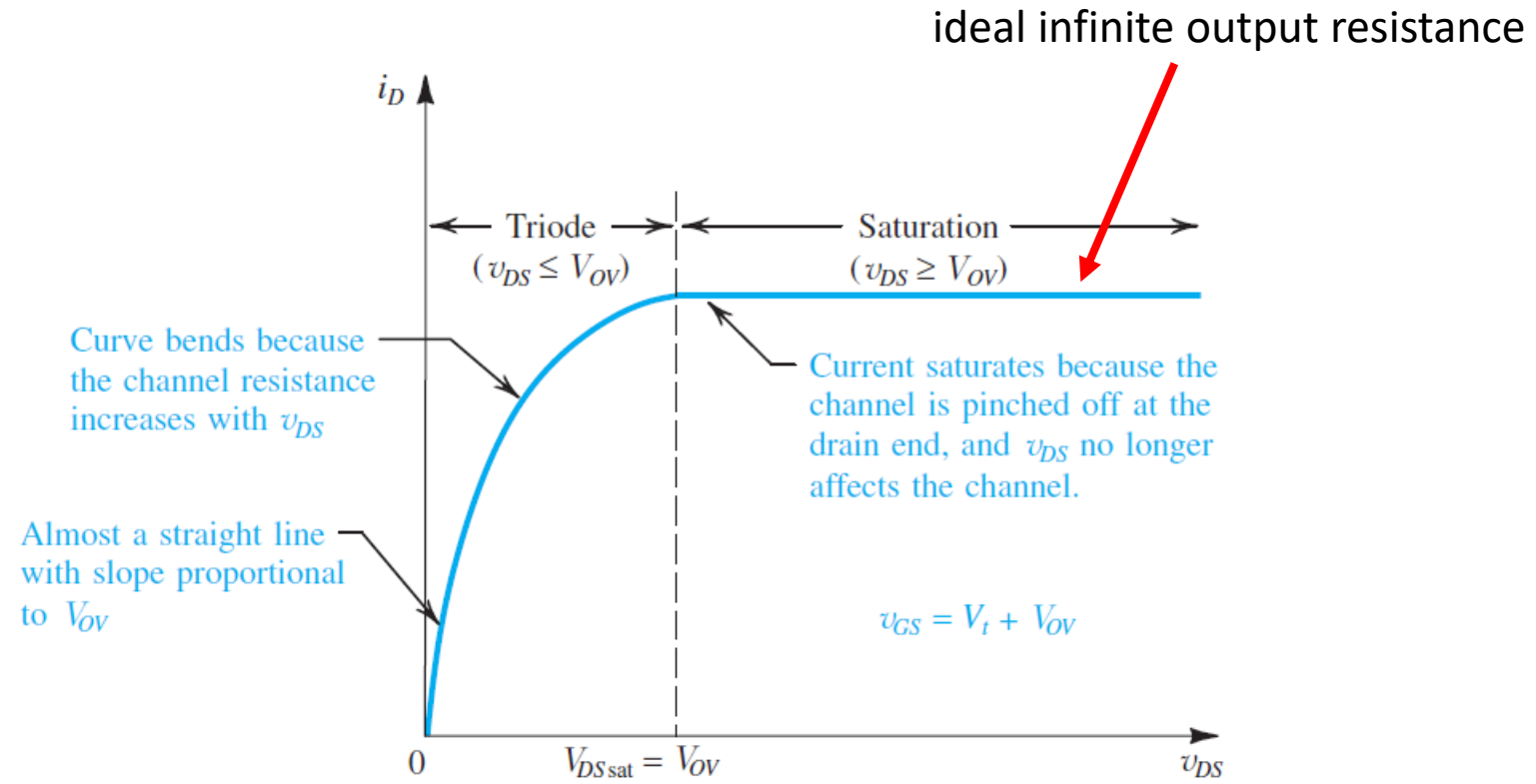
## Finite Output Resistance in Saturation





# Channel-length modulation

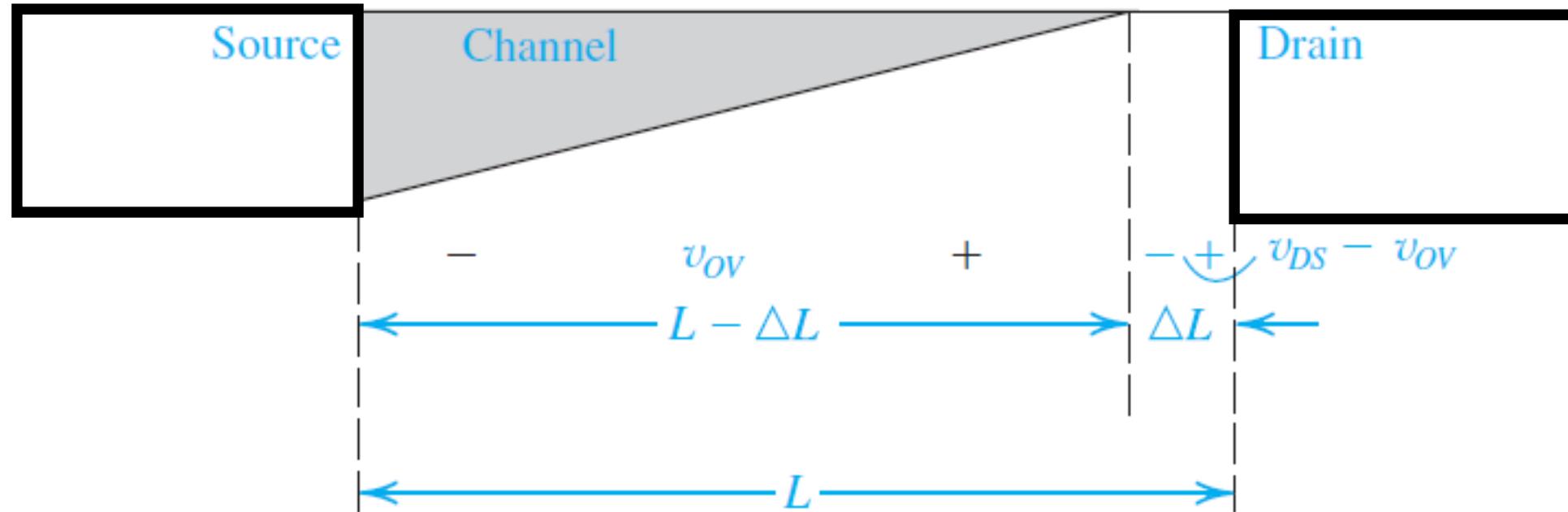


$$i_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (v_{GS} - V_{tn})^2 (1 + \lambda v_{DS})$$



(V<sup>-1</sup>)

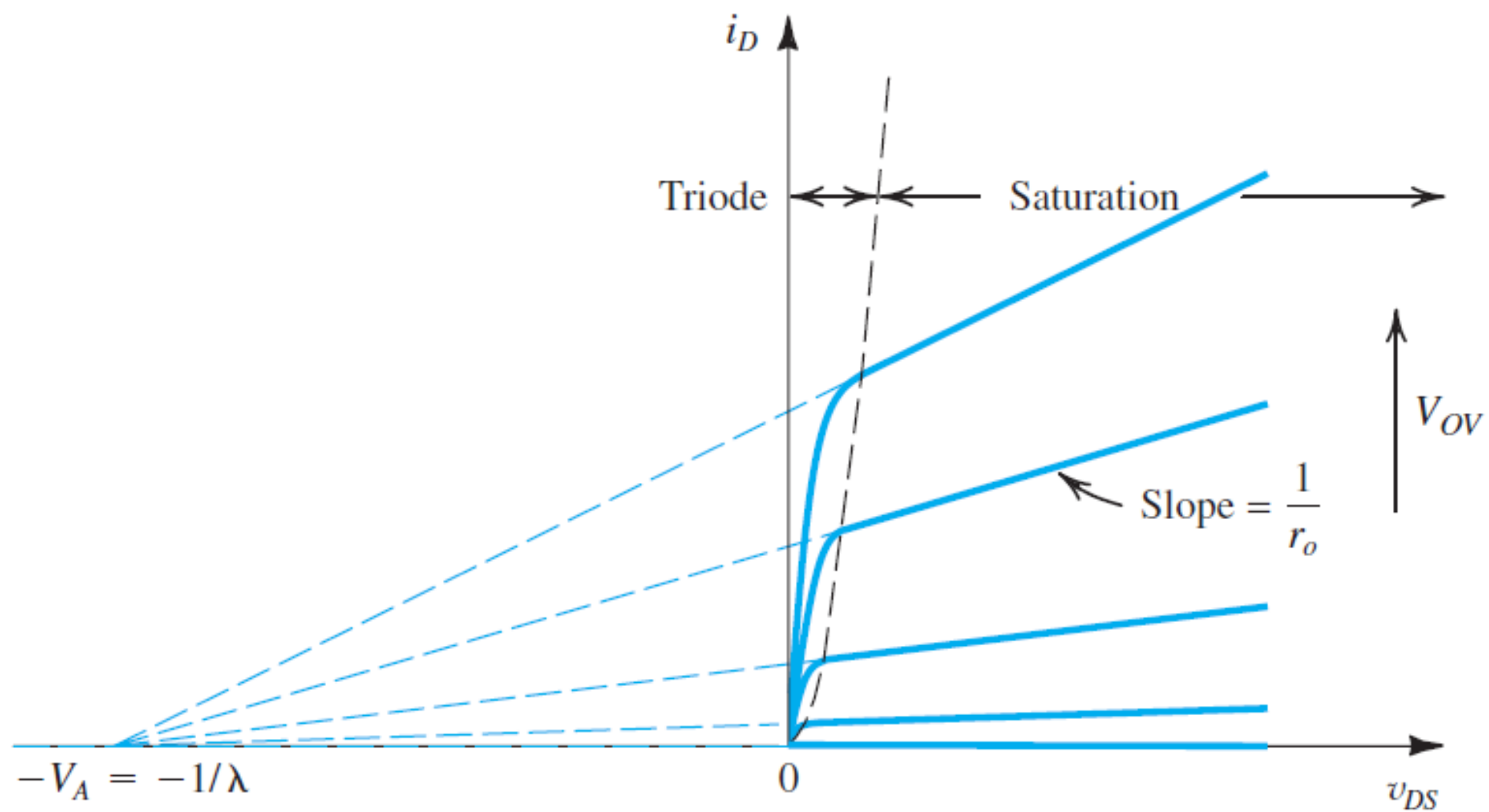“lamda” parameter  
channel-length modulation parameter  
ideal  $\lambda = 0$



Early voltage

$$i_D = \frac{1}{2}k'_n\left(\frac{W}{L}\right)(v_{GS} - V_{tn})^2(1 + \lambda v_{DS})$$

$$r_o \equiv \left[\frac{\partial i_D}{\partial v_{DS}}\right]_{v_{GS} \text{ constant}}^{-1}$$


$$r_o = \left[\lambda \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_{tn})^2\right]^{-1}$$

$$r_o = \frac{1}{\lambda I_D}$$
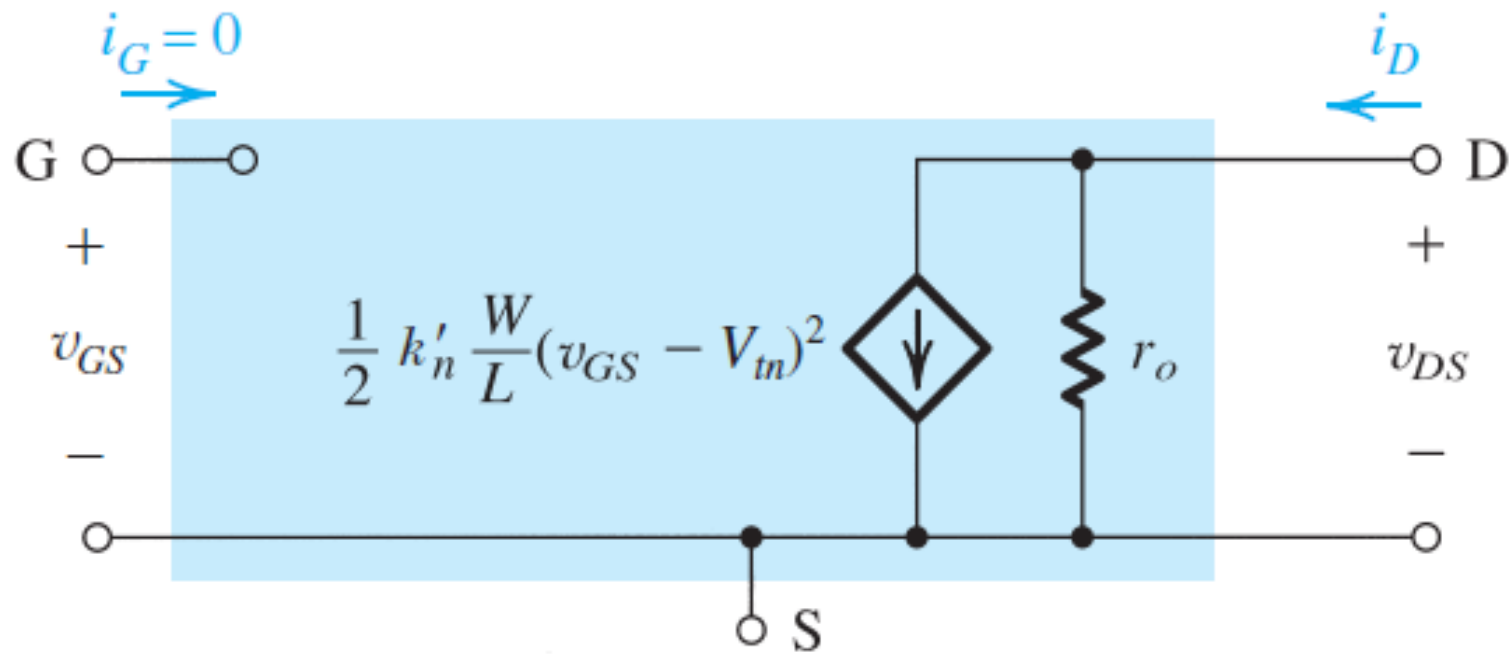
## Transistor model with output resistance



$$r_o = \frac{V_A}{I'_D}$$

$$I'_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_{tn})^2$$




# Modes of Operation

## PMOS

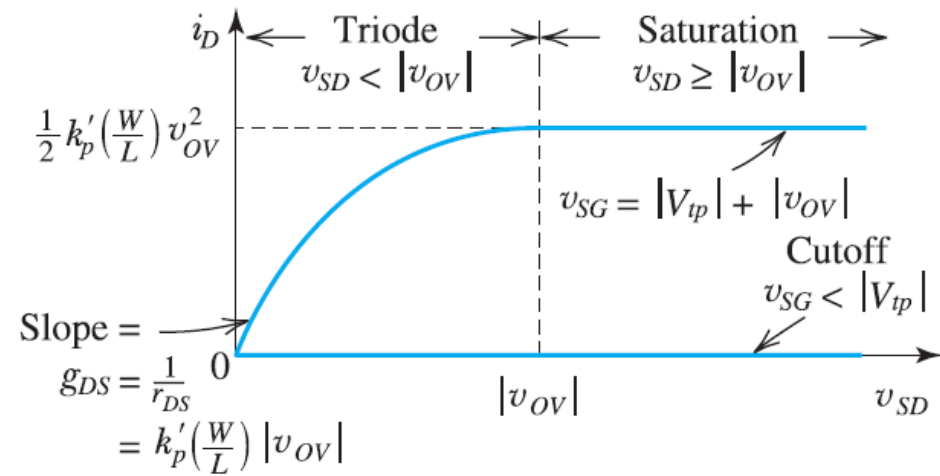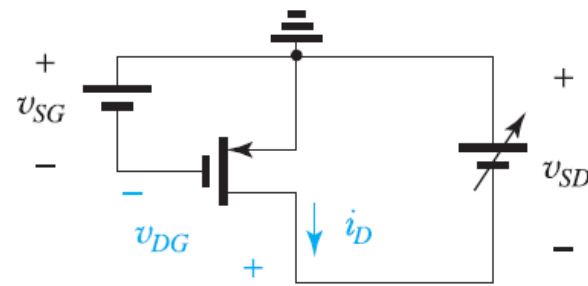

As you study, note voltage polarities and use of absolute values

- $v_{SG} < |V_{tp}|$ : no channel; transistor in cutoff;  $i_D = 0$
- $v_{SG} = |V_{tp}| + |v_{OV}|$ : a channel is induced; transistor operates in the triode region or in the saturation region depending on whether the channel is continuous or pinched off at the drain end;

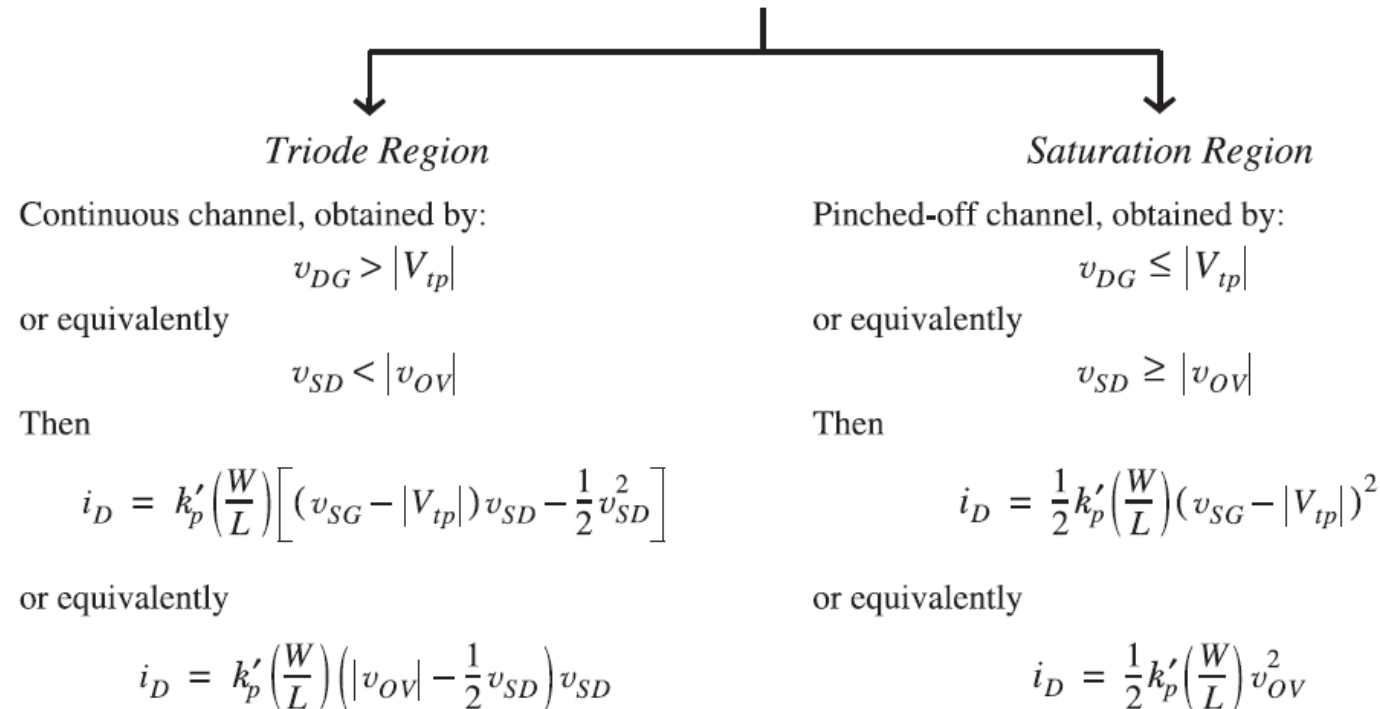


## Channel-length modulation (PMOS)

$$i_D = \frac{1}{2} k'_p \left( \frac{W}{L} \right) (v_{SG} - |V_{tp}|)^2 (1 + |\lambda| v_{SD})$$

$$i_D = \frac{1}{2} k'_p \left( \frac{W}{L} \right) (v_{SG} - |V_{tp}|)^2 \left( 1 + \frac{v_{SD}}{|V_A|} \right)$$



## NMOS

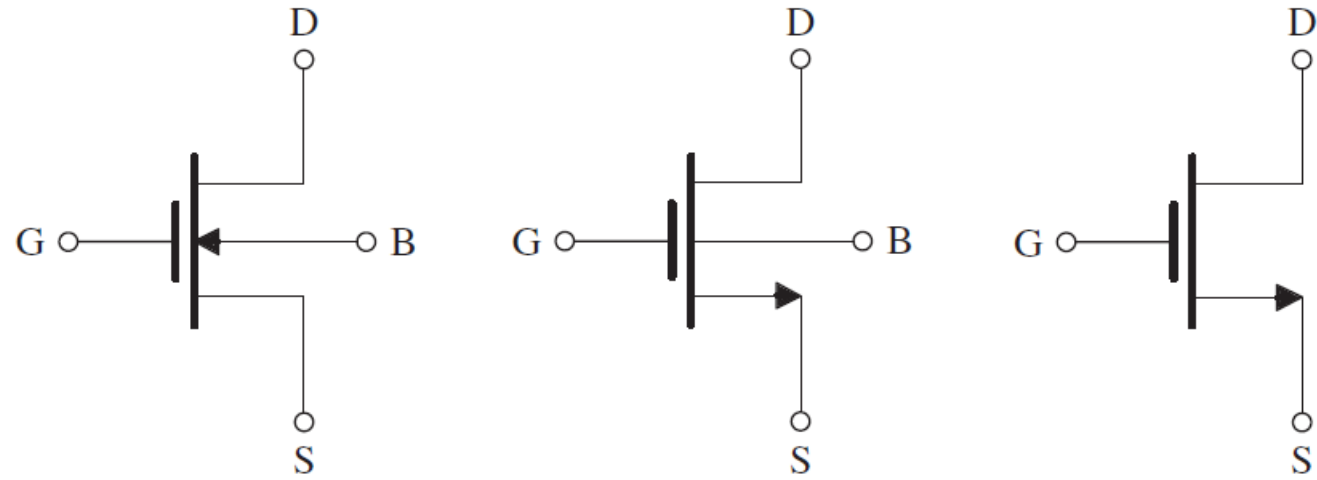

## PMOS

