
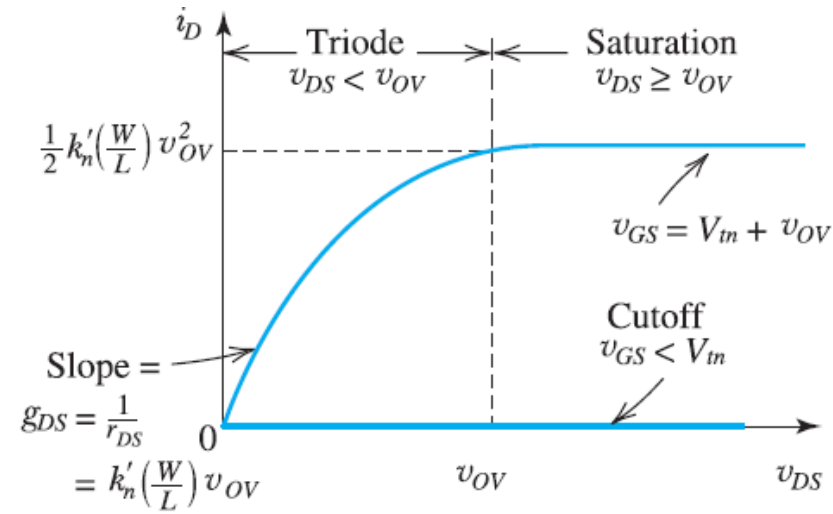


Modes of Operation

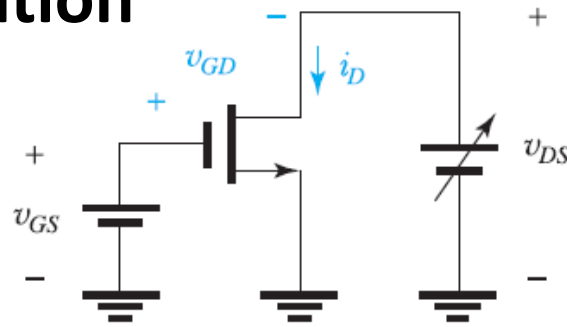

- $v_{GS} < V_{tn}$: no channel; transistor in cutoff; $i_D = 0$
- $v_{GS} = V_{tn} + v_{OV}$: a channel is induced; transistor operates in the triode region or the saturation region depending on whether the channel is continuous or pinched off at the drain end;

Triode Region

Continuous channel, obtained by:

$$v_{GD} > V_{tn}$$

or equivalently:

$$v_{DS} < v_{OV}$$

Then,

$$i_D = k'_n \left(\frac{W}{L} \right) \left[(v_{GS} - V_{tn}) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

or equivalently,

$$i_D = k'_n \left(\frac{W}{L} \right) \left(v_{OV} - \frac{1}{2} v_{DS} \right) v_{DS}$$

Saturation Region

Pinched-off channel, obtained by:

$$v_{GD} \leq V_{tn}$$

or equivalently:

$$v_{DS} \geq v_{OV}$$


Then

$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (v_{GS} - V_{tn})^2$$

or equivalently,

$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) v_{OV}^2$$

i_D vs v_{DS} curves

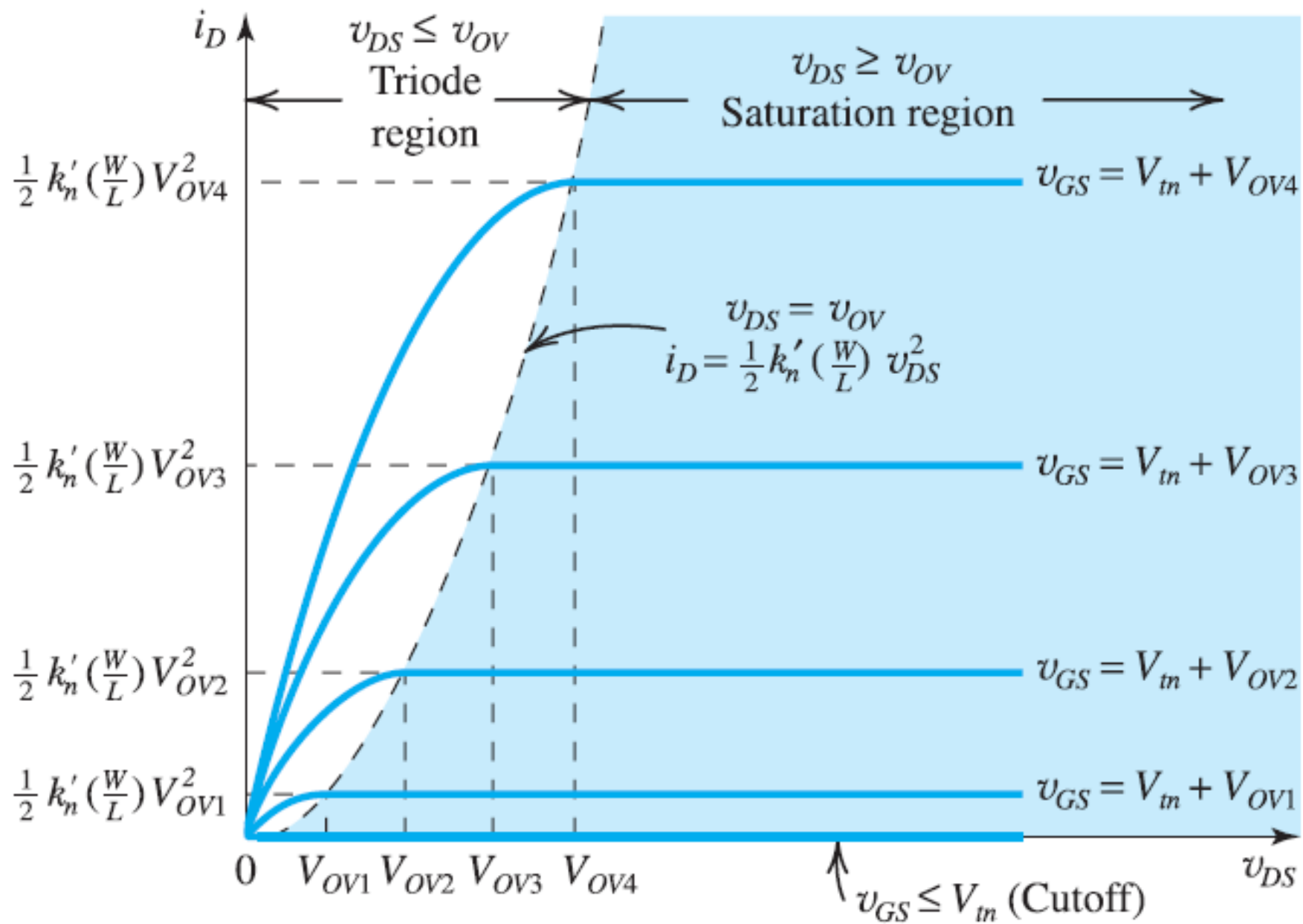

The i_D - v_{GS} Characteristic




Voltage-controlled current source

Saturation current

$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (v_{GS} - V_{tn})^2$$


$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) v_{ov}^2$$

i_D vs v_{GS} curve

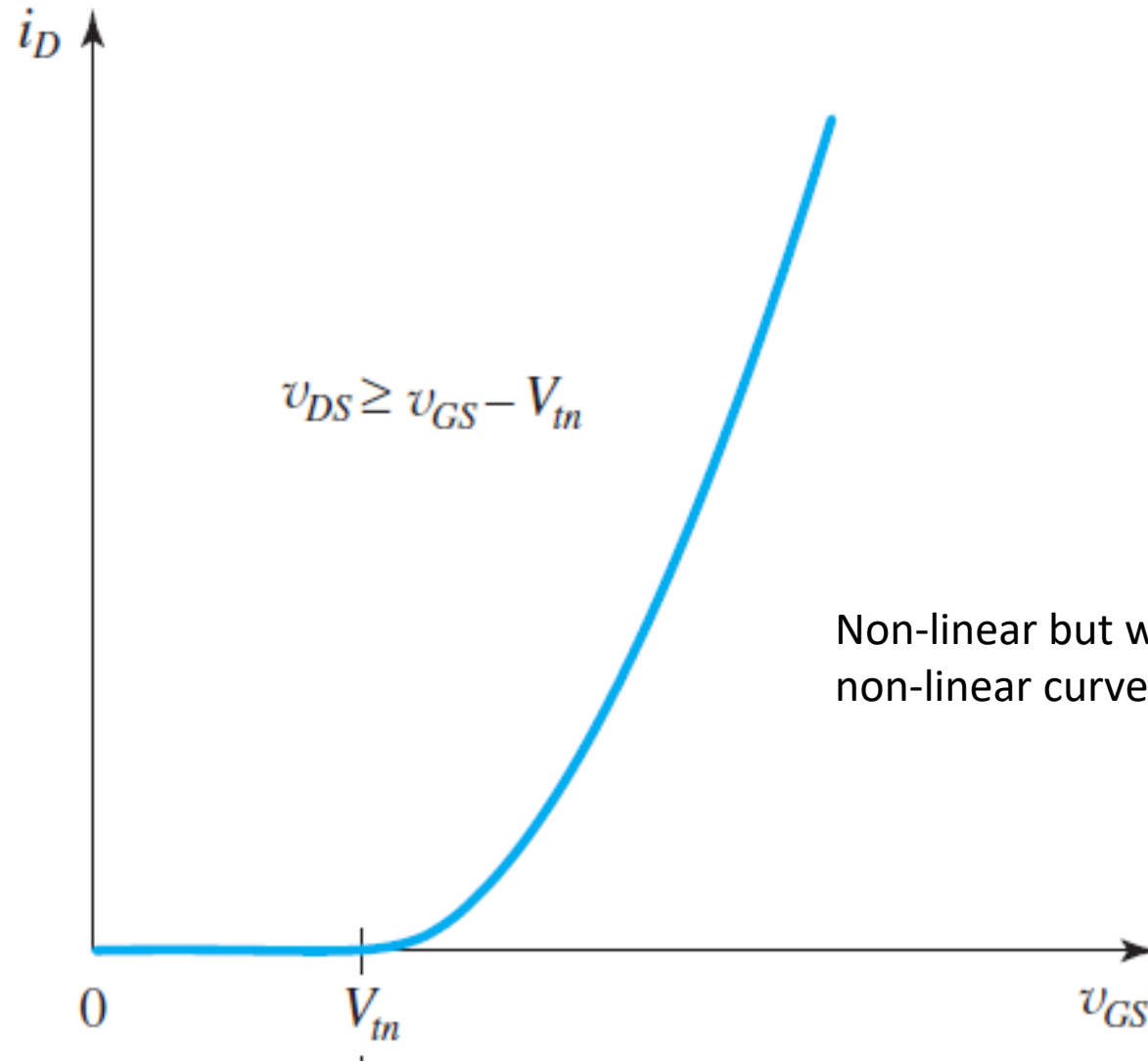


Non-linear but we know what to do with non-linear curves

Large-Signal Model

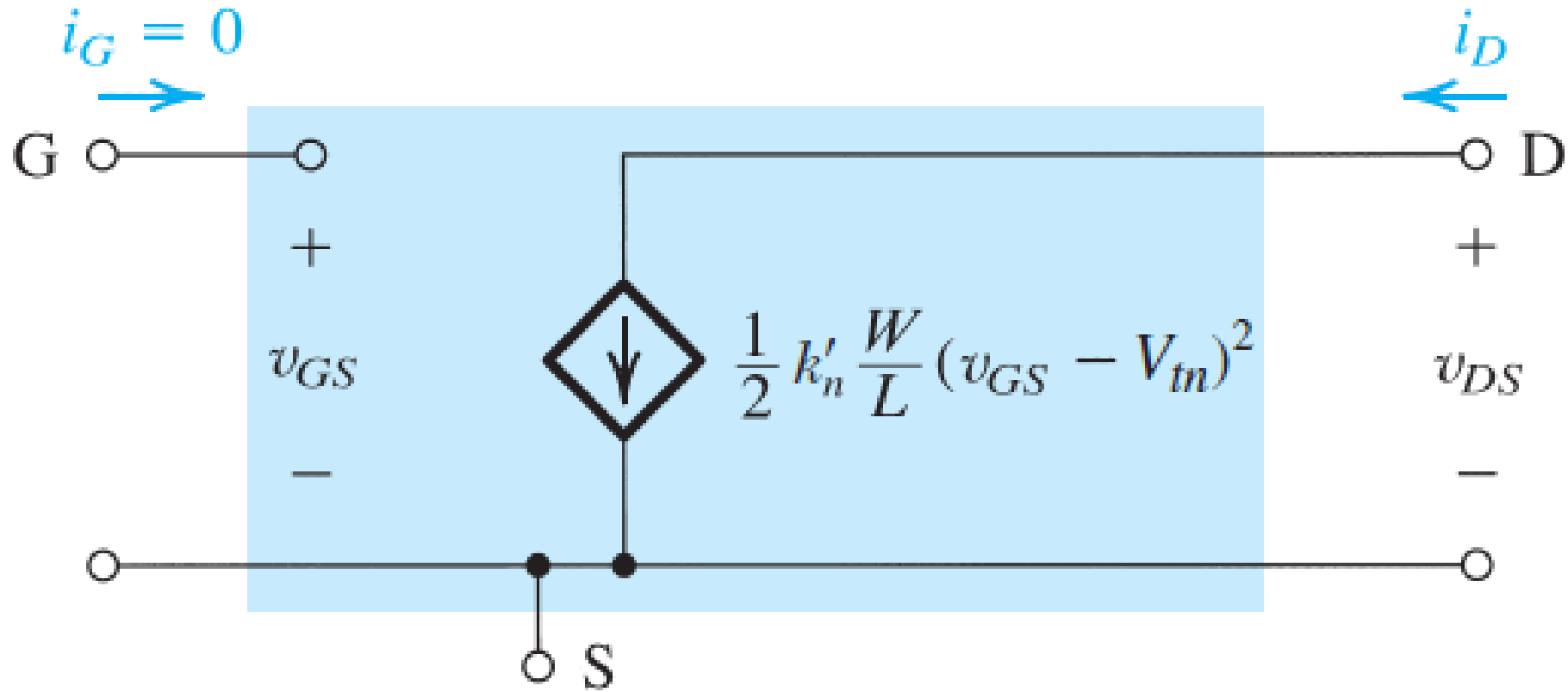


However

Finite Output Resistance in Saturation

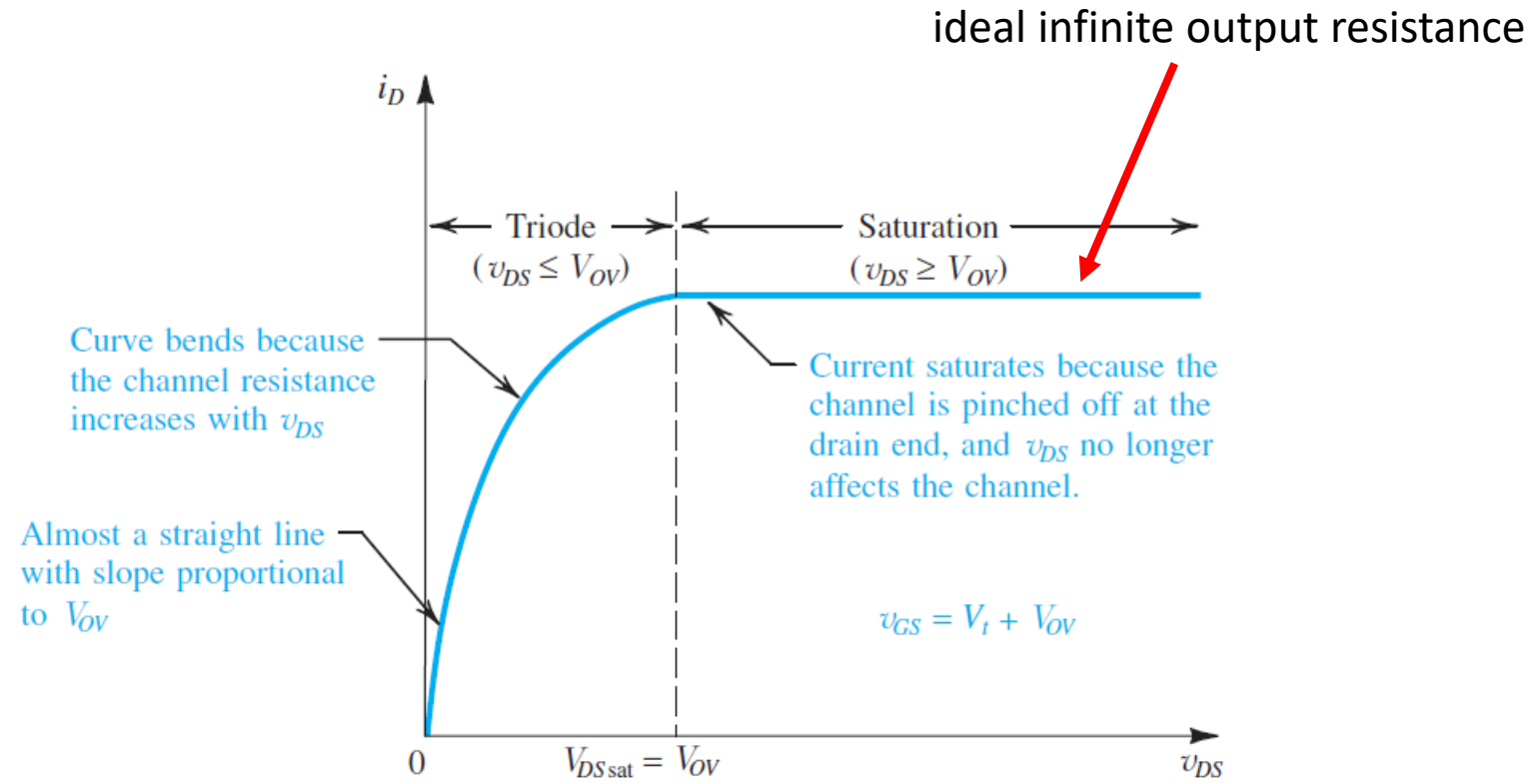

Channel-length modulation

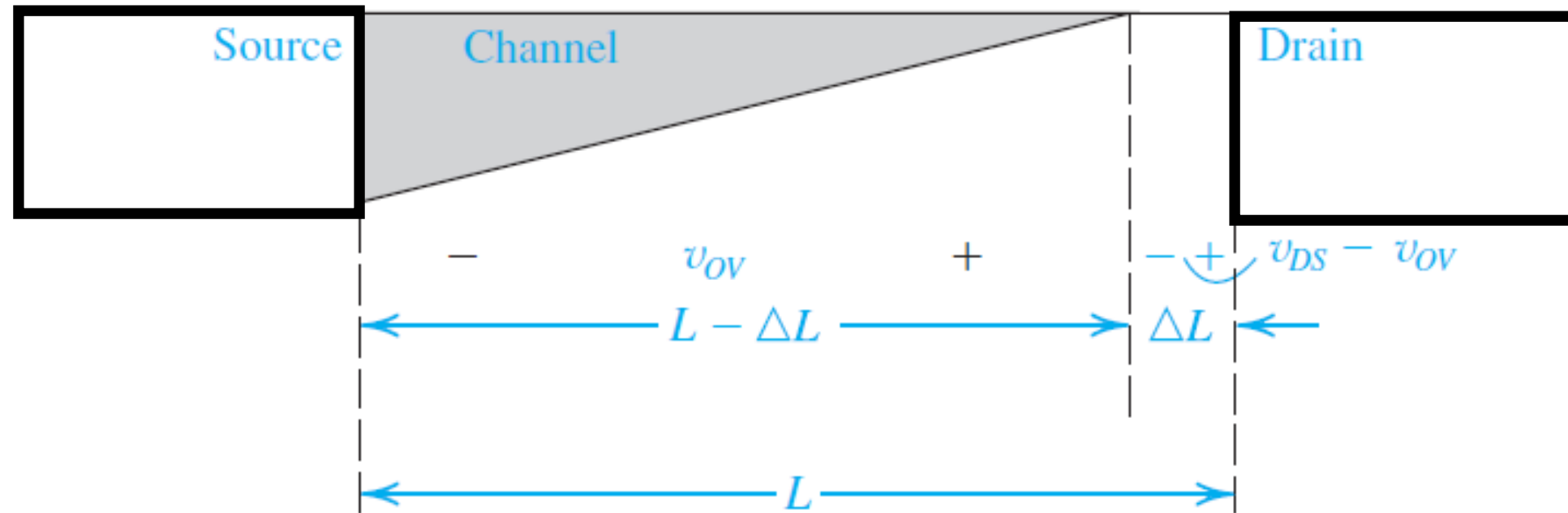

$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (v_{GS} - V_{tn})^2 (1 + \lambda v_{DS})$$



(V⁻¹)

“lamda” parameter
channel-length modulation parameter
ideal $\lambda = 0$

